

WROCLAW UNIVERSITY OF SCIENCE AND TECHNOLOGY
FACULTY OF ELECTRICAL ENGINEERING

Integr. of Distr. Res. in Pow. Lab

Date 03/05/2022

Student name

ID

Gebremeskel Dawit Gebreslassie.....

267607

Lab1 &2 -Load flow in radial network with DER

Table of Contents

1. Exercise aim.....	2
2. Exercise description	2
3. Scheme of analyzed power system	2
4. Calculation of system parameters for given $a=61$	3
5. Input data for $a = 61$	5
6. Load variations results	6
6.1. Load variation result for $0.8 * U$ (8 kv at the load bus)	6
6.2 Load variation for $1*U$ (10 kv at the load bus)	8
6.3. Load variation at 10.5Kv and the effect of Using the generator in bus 4	9
7.Conclusion	11

1. Exercise aim


The aim of this project is to acquire knowledge of the preparation of equivalent parameters of lines, cables and transformers which uses for load flow and voltage analysis for the given radial network in fig.1.

2. Exercise description

The given load variation for the given radial Network is 6 motors start (6S)

Induction motor voltage must not be less than 0.8UN and greater than 10.5 KV at the load bus. In each variation, the node load voltage should be changed to obtain the voltage 1.05UN, i.e., 10.5 kV at the feeder point.

3. Scheme of analyzed power system

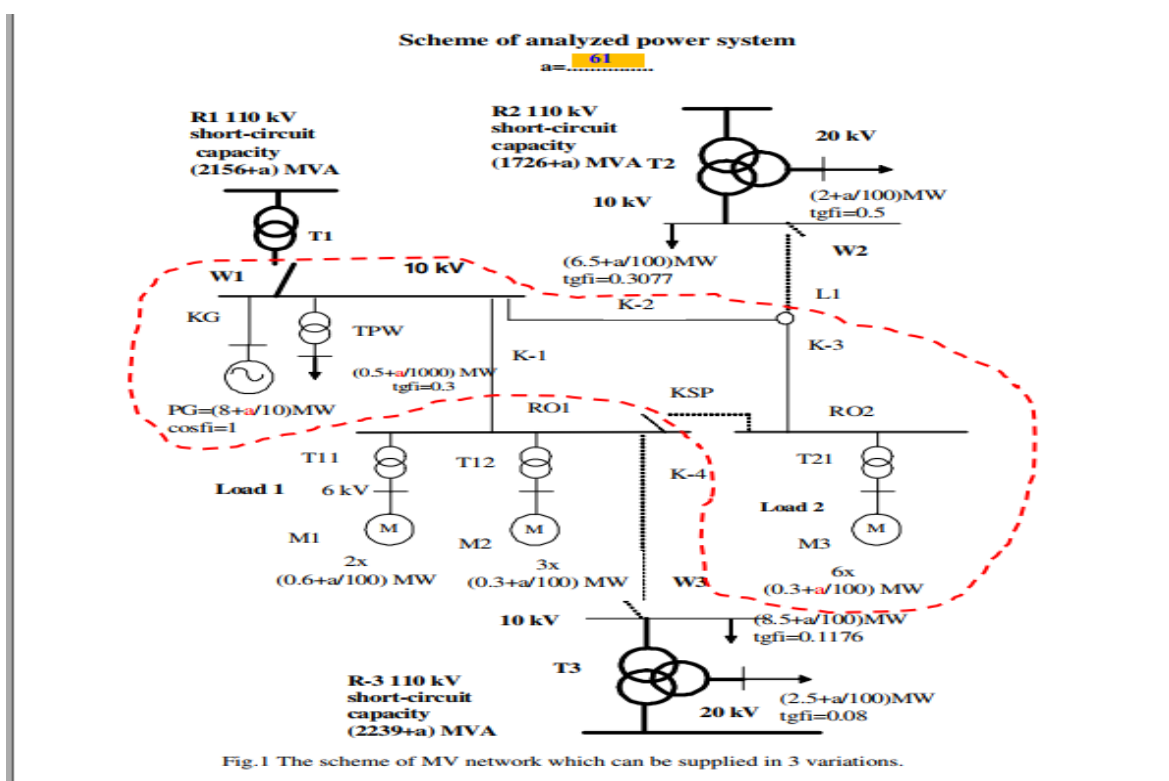

4. Calculation of system parameters for given a=61

1 Calculation of induction motor parameters for a=61
 6 induction motors - 1 pair of poles

$$P_{NM} = \left(0.3 + \frac{a}{100}\right) MW = \left(0.3 + \frac{61}{100}\right) = 0.91 MW$$

$$U_{NM} = 0.5 kV$$

$$\cos \phi_N = \left(0.83 + \frac{a}{1000}\right) = \left(0.83 + \frac{61}{1000}\right) = 0.891$$

$$\cos \phi_K = \left(0.3 + \frac{a}{1000}\right) = \left(0.3 + \frac{61}{1000}\right) = 0.361$$

$$\eta_N = 0.94$$

$$\eta_m = 0.97$$

$$K_{LR} = I_{LR} / I_{Nm} = \left(7 + \frac{a}{100}\right) = \left(7 + \frac{61}{100}\right) = 7.61$$

1 motor nominally loaded

$$P_N = \frac{P_{NM}}{\eta_m} = \frac{0.91 MW}{0.97} = \frac{0.91 MW}{0.97} = 0.938 MW$$

$$S_N = \frac{P_N}{\cos \phi_N} = \frac{0.938 MW}{0.891} = 1.053 MVA$$

1 motor during start

$$\sin \phi_K = \sqrt{1 - \cos^2 \phi_K} = \sqrt{1 - 0.361^2} = 0.9326$$

$$P_K = K_{LR} S_N \cos \phi_K = 7.61 \times 1.053 \times 0.361 = 2.892 MW$$

$$Q_K = K_{LR} S_N \sin \phi_K = 7.61 \times 1.053 \times 0.9326 = 7.47 Mvar$$

⊗ Given Load variation task for me is 6 motors during start (65). So based on the above data we can calculate the total active and reactive power of the load as follows

$$P_{dMW} = 0 \times P_N + 6 \times P_K = 6 \times 2.892 = 17.355 MW$$

$$Q_{dMvar} = 0 \times Q_N + 6 \times Q_K = 6 \times 7.47 = 44.834 Mvar$$

Figure 2: Motor parameter calculation

2 Cable Parameter Calculation for $a = 61$

line K-2 or Cable K-2 Calculation

Al cable $3 \times 240 \text{ mm}^2$, $L = \left(1.7 + \frac{a}{10}\right) \text{ km} = \left(1.7 + \frac{61}{10}\right) = 7.8 \text{ km}$

$R \Rightarrow 1 \text{ km} = 0.128 \Omega$
 $7.8 \text{ km} = ? = \frac{7.8 \text{ km} \times 0.128}{1 \text{ km}} = 0.9984 \Omega$

$X \Rightarrow 1 \text{ km} = 0.08 \Omega$
 $7.8 \text{ km} = ? = \frac{7.8 \text{ km} \times 0.08}{1 \text{ km}} = 0.624 \Omega$

Susceptance $\Rightarrow 1 \text{ km} = 95 \mu\text{S}$
 $7.8 \text{ km} = ? = \frac{7.8 \text{ km} \times 95 \mu\text{S}}{1 \text{ km}} = 741 \mu\text{S}$

* line K-3 or Cable 3 Calculation

Al cable $3 \times 240 \text{ mm}^2 \Rightarrow L = \left(2.13 + \frac{a}{10}\right) = \left(2.13 + \frac{61}{10}\right) = 8.23 \text{ km}$

$R \Rightarrow 1 \text{ km} = 0.128 \Omega$
 $8.23 \text{ km} = ? = \frac{8.23 \text{ km} \times 0.128}{1 \text{ km}} = 1.0534 \Omega$

$X \Rightarrow 1 \text{ km} = 0.08$
 $8.23 \text{ km} = ? = \frac{8.23 \text{ km} \times 0.08}{1 \text{ km}} = 0.6584 \Omega$

Susceptance $\Rightarrow 1 \text{ km} = 95 \mu\text{S}$
 $8.23 \text{ km} = ? = \frac{8.23 \text{ km} \times 95 \mu\text{S}}{1 \text{ km}} = 781.85 \mu\text{S}$

Figure 3: Cable parameter calculation

3 Transformer T_{2L-2} + transformer units for $a = 61$

$$S_N = 3000 \text{ kVA}$$

$$U_K = \left(6 + \frac{a}{100}\right) \% = 6.61 \%$$

$$U_{NH} = 10.5 \text{ kV}$$

$$U_{NL} = 525 \text{ V}$$

$$P_{Cu} = \left(11 + \frac{a}{100}\right) \text{ kW} = 11.61 \text{ kW}$$

$$P_{Fe} = \left(2.1 + \frac{a}{100}\right) \text{ kW} = 2.71 \text{ kW}$$

$$I_0 = \left(1 + \frac{a}{100}\right) \% = 1.61 \%$$

$$U_R = \frac{P_{Cu}}{S_N} \times 100 \% = \frac{11.61 \text{ kW}}{3000 \text{ kVA}} \times 100 \% = 0.387 \%$$

$$U_X = \sqrt{U_K^2 - U_R^2} = \sqrt{6.61^2 - 0.387^2} = 6.598$$

$$R_T = \frac{\frac{U_R}{100} \times \frac{U_{NH}^2}{\frac{S_N}{1000}}}{2} = \frac{0.387}{100} \times \frac{10.5^2 \text{ MV}^2}{3 \text{ MVA}} = \frac{0.1422}{2} = 0.0711 \Omega$$

$$X_T = \frac{\frac{U_X}{100} \times \frac{U_{NH}^2}{\frac{S_N}{1000}}}{2} = \frac{6.598}{100} \times \frac{10.5^2 \text{ MV}^2}{3 \text{ MVA}} = \frac{1.2125}{2} = 1.2125 \Omega$$

$$G_T = \frac{P_{Fe}}{U_{NH}^2} = \frac{2.71 \text{ kVA}}{(10.5 \text{ kV})^2} = 49.161 \mu\text{S}$$

$$B_T = \frac{I_0}{100} \cdot \frac{S_N}{U_{NH}^2} = \frac{1.61}{100} \times \frac{3000 \text{ kVA}}{(10.5 \text{ kV})^2} = 876.19 \mu\text{S}$$

Figure 4: Transformer parameter calculation

5. Input data for $a = 61$

```
function [nodes,branches,UN,U]=erlfd61
UN=10.0; % nominal voltage of equivalent network
U =10.0; % voltage set at the load bus
%
nodes=
```

```

% Pd(+) - active load at node,
% Pd(-) - active injection at node
% Qd(+) - reactive load at node (inductive),
% Qd(-) - reactive injection at node (capacitive)
% Un_kV - nominal voltage of equivalent network
% Uk_st - voltage angle / zero before cload flow computing/
%Node   Un_kV   Uk_st   Pd_MW   Qd_Mvar
% 1      2      3      4      5
% 1  10.00   0      17.355  44.834
% 2  10.00   0       0       0
% 3  10.00   0       0       0
% 4  10.00   0       0       0
];
%
%
%
branches=[
% k - node number at pi-end, p - node number at pi-begin
% Sp=Pp+jQp--->p____R____X____k----> Sk=Pk+jQk
% Up/Ukp      |          |      Uk/Ukk
%              Yp        Yk
%              |          |
% -----
%
% R - resistance, X - reactance
% Yp=G/2+jB/2 - shunt admittance at pi-begin
% Yk=G/2+jB/2 - shunt admittance at pi-end
% NOTE! B>0 for line and B<0 for transformer
% Give G,B w mikrosimens with proper sign:
% (-)minus for transformer,
% (+)plus for line
% Program creates pi-circuit with G/2 and B/2 so give G nad B.
% p   k   R_om      X_om      G_mikroS      B_mikroS
% 1   2   3         4         5         6
% 2   1  0.071111   1.2125   49.161      -876.19
% 3   2  1.0534     0.6584     0        781.85
% 4   3  0.9984     0.624      0        741
];
%

return;

```

6. Load variations results

6.1. Load variation result for $0.8 * U$ (8 kv at the load bus)

```
>> erlf
```

```
plikdat =
```

```
'erlfd61'
```

% Calculation stop: 2022- 5- 4 godz. 10h, 7min, 9.88s

Number of pi-circuits np_i = 3

Total bus number n = 4

Nominal voltage of equivalent network UN = 10.000 kV

Voltage set at load bus U = 8.000 kV

czwornik 2 - 1

Up_kV	Ukp_st	Pp_MW	dPp_MW	Qp_Mvar	dQp_Mvar	Uk_kV	Ukk_st	Pk_MW	dPk_MW	Qk_Mvar	dQk_Mvar
15.111	8.5	19.9275	0.0056	88.447	-0.1000	8.000	0.0	17.3550	0.0016	44.834	-0.0280

czwornik 3 - 2

Up_kV	Ukp_st	Pp_MW	dPp_MW	Qp_Mvar	dQp_Mvar	Uk_kV	Ukk_st	Pk_MW	dPk_MW	Qk_Mvar	dQk_Mvar
21.027	-6.1	57.7759	0.0000	111.841	-0.1728	15.111	8.5	19.9275	0.0000	88.447	-0.0893

czwornik 4 - 3

Up_kV	Ukp_st	Pp_MW	dPp_MW	Qp_Mvar	dQp_Mvar	Uk_kV	Ukk_st	Pk_MW	dPk_MW	Qk_Mvar	dQk_Mvar
27.321	-13.6	93.4781	0.0000	133.715	-0.2766	21.027	-6.1	57.7759	0.0000	111.841	-0.1638

node	UN_kV	U_kV	dU_%	Uk_st	P_MW	Q_MW
1	10.000	8.000	0.0	0.0	17.3550	44.8340
2	10.000	15.111	51.1	8.5	19.9275	88.4473
3	10.000	21.027	110.3	-6.1	57.7759	111.8414
4	10.000	27.321	173.2	-13.6	93.4781	133.7149

Active losses P_{str} = 76.123 MW

Transmission efficiency eta = 18.566 %

End of calculation by erlf.m - see results in file erlfout.m>>

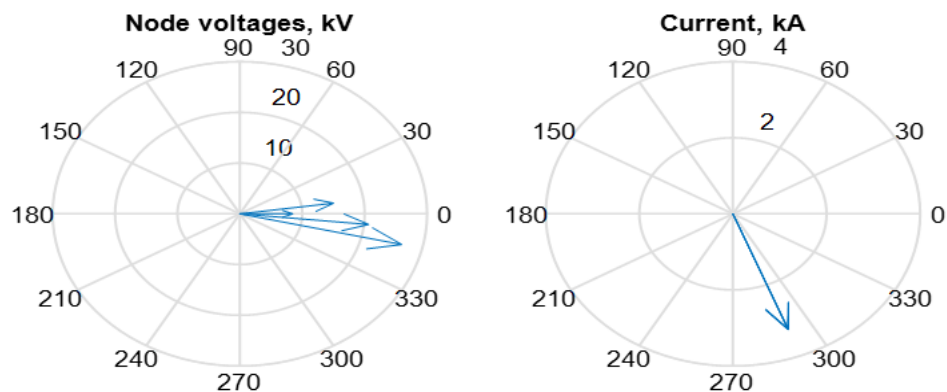


Figure 5: Node voltage and current results for 8 KV

6.2 Load variation for 1*U (10 kv at the load bus)

```
>> erlf
```

```
plikdat =
```

```
'erlfd61'
```

```
% Calculation stop: 2022- 5- 2 godz. 12h, 41min, 18.75s
```

```
Number of pi-circuits      npi = 3
```

```
Total bus number          n = 4
```

```
Nominal voltage of equivalent network UN = 10.000 kV
```

```
Voltage set at load bus    U = 10.000 kV
```

```
czwornik 2 - 1
```

```
Up_kV Ukp_st Pp_MW dPp_MW Qp_Mvar dQp_Mvar Uk_kV Ukk_st Pk_MW dPk_MW  
Qk_Mvar dQk_Mvar  
15.656 6.6 19.0043 0.0060 72.661 -0.1074 10.000 0.0 17.3550 0.0025 44.834 -  
0.0438
```

```
czwornik 3 - 2
```

```
Up_kV Ukp_st Pp_MW dPp_MW Qp_Mvar dQp_Mvar Uk_kV Ukk_st Pk_MW dPk_MW  
Qk_Mvar dQk_Mvar  
20.399 -5.0 43.1850 0.0000 87.516 -0.1627 15.656 6.6 19.0043 0.0000 72.661 -  
0.0958
```

```
czwornik 4 - 3
```

```
Up_kV Ukp_st Pp_MW dPp_MW Qp_Mvar dQp_Mvar Uk_kV Ukk_st Pk_MW dPk_MW  
Qk_Mvar dQk_Mvar  
25.358 -11.7 65.9701 0.0000 101.364 -0.2382 20.399 -5.0 43.1850 0.0000 87.516 -  
0.1542
```

```
node UN_kV U_kV dU_% Uk_st P_MW Q_MW
```

```
1 10.000 10.000 0.0 0.0 17.3550 44.8340
```

```
2 10.000 15.656 56.6 6.6 19.0043 72.6605
```

```
3 10.000 20.399 104.0 -5.0 43.1850 87.5155
```

```
4 10.000 25.358 153.6 -11.7 65.9701 101.3638
```

```
Active losses Pstr = 48.615 MW
```

```
Transmission efficiency eta = 26.307 %
```

```
End of calculation by erlf.m - see results in file erlfout.m>>
```

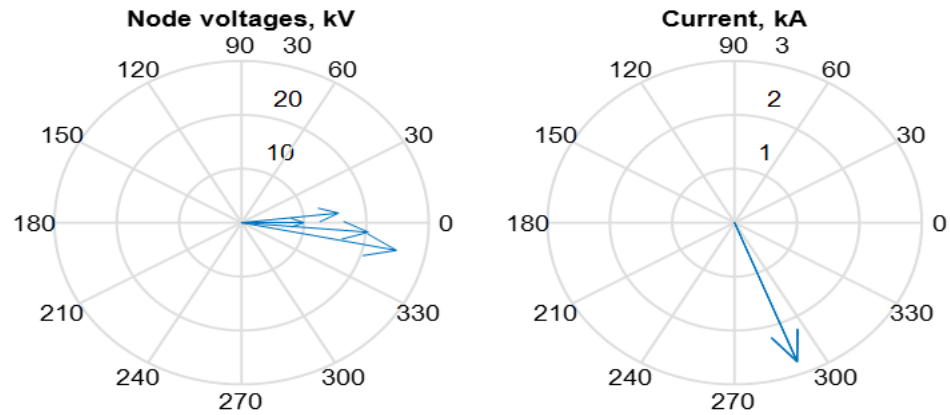



Figure 6: Node voltage and current results for 10 KV

6.3. Load variation at 10.5KV and the effect of Using the generator in bus 4

```
>> erlf
```

```
plikdat =
```

```
'erlfd61'
```

```
% Calculation stop: 2022- 5- 4 godz. 9h, 31min, 22.93s
```

```
Number of pi-circuits      npi = 3
```

```
Total bus number          n = 4
```

```
Nominal voltage of equivalent network UN = 10.000 kV
```

```
Voltage set at load bus    U = 10.500 kV
```

```
czwornik 2 - 1
```

Up_kV	Ukp_st	Pp_MW	dPp_MW	Qp_Mvar	dQp_Mvar	Uk_kV	Ukk_st	Pk_MW	dPk_MW	Qk_Mvar	dQk_Mvar
-------	--------	-------	--------	---------	----------	-------	--------	-------	--------	---------	----------

15.881	6.1	18.8520	0.0062	70.048	-0.1105	10.500	0.0	17.3550	0.0027	44.834	-0.0483
--------	-----	---------	--------	--------	---------	--------	-----	---------	--------	--------	---------

```
czwornik 3 - 2
```

Up_kV	Ukp_st	Pp_MW	dPp_MW	Qp_Mvar	dQp_Mvar	Uk_kV	Ukk_st	Pk_MW	dPk_MW	Qk_Mvar	dQk_Mvar
20.399	-4.8	40.7736	0.0000	83.488	-0.1627	15.881	6.1	18.8520	0.0000	70.048	-0.0986

czwornik 4 - 3

Up_kV	Ukp_st	Pp_MW	dPp_MW	Qp_Mvar	dQp_Mvar	Uk_kV	Ukk_st	Pk_MW	dPk_MW	Qk_Mvar	dQk_Mvar
25.104	-11.2	61.4238	0.0000	96.006	-0.2335	20.399	-4.8	40.7736	0.0000	83.488	-0.1542

node	UN_kV	U_kV	dU_%	Uk_st	P_MW	Q_MW
1	10.000	10.500	0.0	0.0	17.3550	44.8340
2	10.000	15.881	58.8	6.1	18.8520	70.0475
3	10.000	20.399	104.0	-4.8	40.7736	83.4878
4	10.000	25.104	151.0	-11.2	75.5238	96.0065

Active losses Pstr = 44.069 MW

Transmission efficiency eta = 41.649 %

End of calculation by erlf.m - see results in file erlfout.m>>

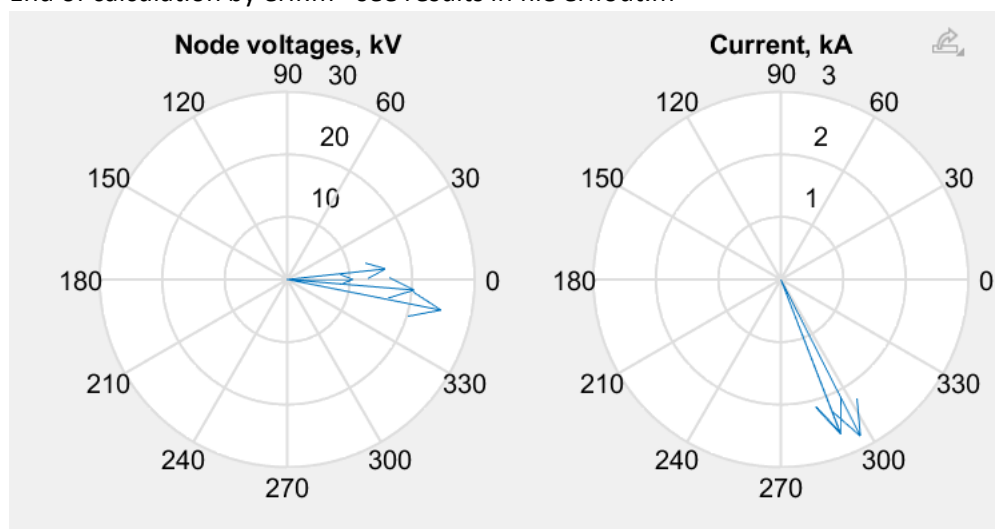


Figure 7: Node voltage and current results for 10.5 KV

7.Conclusion

Three different cases are selected to perform this task at the given load.

- The first case is performed at 8Kv at the load bus. At this voltage level, the active power losses is 76.123 MW, and transmission efficiency is 18.566 %
- The second case is performed for 10Kv load bus. At this voltage level, the active power losses is 48.615 MW and transmission efficiency is 26.307 %
- The third case is performed for 10.5Kv at load bus and with the generator in bus 4 operating to increase the efficiency. at this voltage level, the active power losses is 44.069 MW and transmission efficiency is 41.649 %. since the generator in bus 4 is operating, the transmission efficiency has improved a lot comparing with the other two cases.

An important point to note is, as the voltage in the load bus increases the transmission efficiency increases and the active power loss decreases. So, we have two methods to increase the transmission efficiency: by using the generator in bus 4 and by increasing the Load bus voltage.

In summary, it is observed that as the load varies the receiving end voltage varies. Moreover, getting a 10.5Kv supply voltage is impossible due to the very high reactive power demand since all 6 motors are starting in this case, which requires 17.355Mw active and 44.834 Mvar reactive power. This very high reactive power demand shows that a very high voltage is required to increase the transmission efficiency and decrease the active losses. However, we cannot increase the voltage in the load bus as we want since it demands a high voltage in the supply.